

Name: Maaz Habib

Registration NO:20PWCSE1952

Total number of pages:6

MID TERM PAPER

MaaZ Habib
20PWCSE1952

Pgs-1

Q3) Bicycle are convenient 16W and 110V to the e-bike.

Solutions:-

For e-bike the required power and voltage are;

$$\text{Power, } P = 16 \text{ W}$$

$$\text{Voltage, } V = 110 \text{ V}$$

Also,

$$\text{batteries} = 12 \text{ V}$$

$$\text{resistors} = \text{Any value}$$

First we need to find current "I"

As, we know that

$$P = VI$$

$$I = P/V$$

$$I = \frac{16 \text{ W}}{110 \text{ V}}$$

$$I = 0.145 \text{ A}$$

Now taking 10 batteries of 12V and we connect them in series


(P.T.O)

Maa Z Habib
20PWCSE1952

pg 8-101

Day M T W T F S

Date / /

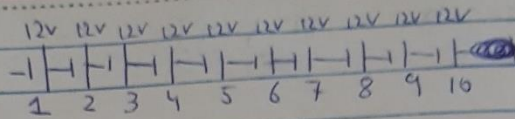

We know that in series voltage is added, so,

∴ Total voltage = 120V

As,

Given in Question e-bike
requires 110V, Dropping 10V by
resistor,

Value of R;

$$V = IR$$


$$R = \frac{V}{I}$$

$$V = 10$$

$$I = 0.145A$$

$$R = \frac{10}{0.145}$$

$$R = 68.96\Omega$$

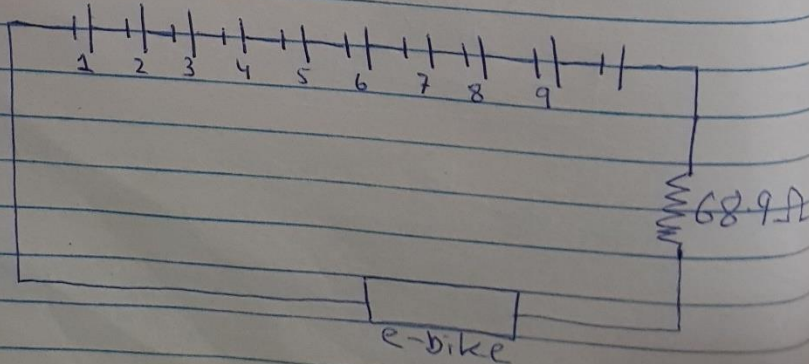


Maaaz Habib
20PWCSE1952

Pg: (2)

Q1) The circuit of figure 1..... figure 1 is
2.5A.

Solr

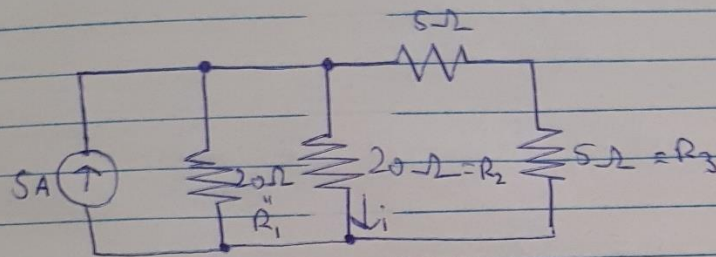

Given:

$$R_1 = 20\Omega$$

$$R_2 = 20\Omega$$

$$R_3 = 5\Omega + 5\Omega = 10\Omega$$

By formula we know that

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$1 = \frac{1}{20} + \frac{1}{20} + \frac{1}{10}$$

$$1 = \frac{1+1+2}{20}$$

$$1 = \frac{4}{20} \times 5$$

$$1 = \frac{1}{5}$$

Reciporcalling

$$R_{eq} = 5$$

Now using current divider formula

$$i = i_T \times \frac{R_{eq}}{R_i}$$

So, here,

$$i_T = 5A$$

$$R_{eq} = 5\Omega$$

$$R_i = 20\Omega$$

putting values we get

$$i = 5 \times \frac{5}{20}$$


$$i = \frac{25}{20}$$

$$i = 5/4$$

$$i = 1.25A$$

In textbook there is an error as $i = 1.25A$ and $i \neq 2.5A$

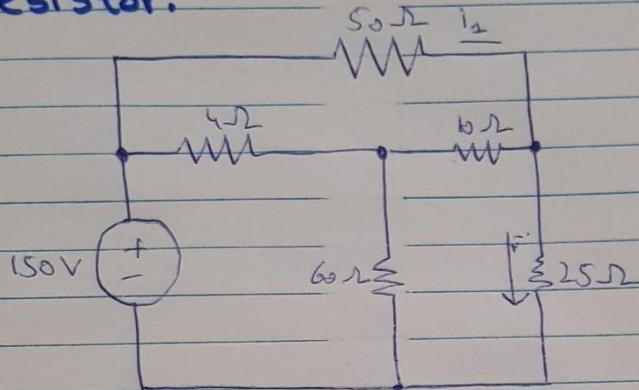Q2) consider the circuit in the 50Ω resistor.



As we know that

$$P = VI$$

Also,

voltage drop

$$V = IR$$

here $V = 50V$

So,

$$P = \frac{V^2}{R}$$

$$P = \frac{(50)^2}{50}$$

$$P = \frac{50 \times 50}{50}$$

$$P = 50 \text{ Watt} \text{ Ans}$$