

Chapter 28 Examples:

By = MaaZ Habib

To = Haseen Ullah Jan

Sec = CSE/C

Example 28.1:-

A battery of 3.00Ω

Solution: (A)

$$I = \frac{\mathcal{E}}{R+r} = \frac{12.0V}{(3.00\Omega + 0.05\Omega)} = \boxed{3.93A}$$

$$\Delta V = \mathcal{E} - Ir = 12.0 - (3.93)(0.05)\Omega = \boxed{11.8V}$$

$$\Delta V = IR = (3.93A)(3.00\Omega) = \boxed{11.8V}$$

(B): calculate battery.

$$P_R = I^2 R = (3.93A)^2 (3.00\Omega) = \boxed{46.3W}$$

$$P_r = I^2 r = (3.93A)^2 (0.05\Omega) = \boxed{0.772W}$$

$$P = P_R + P_r = 46.3W + 0.772W = \boxed{47.1W}$$

Example 28.2:-

Find Active figure.

Solution:-

$$(1) \quad P = I^2 R = \frac{\mathcal{E}^2 R}{(R+r)^2}$$

$$\frac{dP}{dR} = \frac{d}{dR} \left[\frac{\mathcal{E}^2 R}{(R+r)^2} \right] = \frac{d}{dR} [\mathcal{E}^2 R (R+r)^{-2}] = 0$$

$$[\varepsilon^2 (R+r)^{-2}] + [\varepsilon^2 R (-2) (R+r)^{-3}] = 0$$

$$\frac{\varepsilon^2 (R+r)}{(R+r)^3} - \frac{2\varepsilon^2 R}{(R+r)^3} = \frac{\varepsilon^2 (r-R)}{(R+r)^3} = 0$$

$$\boxed{R=r}$$

example 22.4:

Four show in fig.

Solution (A):

$$R_{eq} = 8.0 \Omega + 4.0 \Omega = 12.0 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{6.0 \Omega} + \frac{1}{3.0 \Omega} = \frac{3}{6.0 \Omega}$$

$$R_{eq} = 2.0 \Omega$$

$$R_{eq} = 12.0 \Omega + 2.0 \Omega = \boxed{14.0 \Omega}$$

(B) what between a and c?

$$I = \frac{\Delta V_{ac}}{R_{eq}} = \frac{42V}{14.0 \Omega} = \boxed{3.0A}$$

$$\Delta V_1 = \Delta V_2 \rightarrow (6.0 \Omega) I_1 = (3.0 \Omega) I_2 \rightarrow I_2 = 2I_1$$

$$I_1 + I_2 = 3.0A \rightarrow I_1 + 2I_1 = 3.0A \rightarrow \boxed{I_1 = 1.0A}$$

$$I_2 = 2I_1 \rightarrow 2(1.0A) = \boxed{2.0A}$$

example 28.5:-

Three point a and b.

Solution:- (A) :-

$$\frac{1}{R_{eq}} = \frac{1}{3.00\Omega} + \frac{1}{6.00\Omega} + \frac{1}{9.00\Omega} = \frac{11.0}{18.0\Omega}$$

$$R_{eq} = \frac{18.0\Omega}{11.0} = \boxed{1.64\Omega}$$

(B) Find the current in each resistor.

$$I_1 = \frac{\Delta V}{R_1} = \frac{18.0V}{3.00\Omega} = \boxed{6A}$$

$$I_2 = \frac{\Delta V}{R_2} = \frac{18.0V}{6.00\Omega} = \boxed{3A}$$

$$I_3 = \frac{\Delta V}{R_3} = \frac{18.0V}{9.00\Omega} = \boxed{2A}$$

(C) calculate of resistors:

$$3\Omega : P_1 = I_1^2 R_1 = (6A)^2 (3\Omega) = \boxed{108W}$$

$$6\Omega : P_2 = I_2^2 R_2 = (3A)^2 (6\Omega) = \boxed{54W}$$

$$9\Omega : P_3 = I_3^2 R_3 = (2A)^2 (9\Omega) = \boxed{36W}$$

example 28.6:-

A single circuit.

Solution:-

$$\Sigma \Delta V = 0 \rightarrow \mathcal{E}_1 - IR_1 - \mathcal{E}_2 - IR_2 = 0$$

$$(1) I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2} = \frac{6.0V - 12V}{8.0\Omega + 6\Omega} = \boxed{-0.33A}$$

(P.T.O)

example 28-7:-

Find shown in fig.

Solution:-

$$1) I_1 + I_2 - I_3 = 0$$

$$2) \begin{matrix} 10.0V \\ \downarrow \text{abeda} \end{matrix} - (6.0\Omega)I_1 - (2.0\Omega)I_3 = 0$$

$$\bullet \text{ befcb} \rightarrow -(4.0\Omega)I_2 + 14.0V + (6.0\Omega)I_1 - 10.0V = 0$$

$$3) -24.0V + (6.0\Omega)I_1 - (4.0\Omega)I_2 = 0$$

$$10.0V - (6.0\Omega)I_1 - (2.0\Omega)(I_1 + I_2) = 0$$

$$4) 10.0V - (8.0\Omega)I_1 - (2.0\Omega)I_2 = 0$$

$$5) -96.0V + (24.0\Omega)I_1 - (16.0\Omega)I_2 = 0$$

$$6) 30.0V - (24.0\Omega)I_1 - (6.0\Omega)I_2 = 0$$

$$-66.0V - (22.0\Omega)I_2 = 0$$

$$\boxed{I_2 = -3.0A}$$

$$-24.0V + (6.0\Omega)I_1 - (4.0\Omega)(-3.0A) = 0$$

$$-24.0V + (6.0\Omega)I_1 + 12.0V = 0$$

$$\boxed{I_1 = 2.0A}$$

$$I_3 = I_1 + I_2 = 2.0A - 3.0A = \boxed{-1.0A}$$

example 28.8:-

Many capacitor?

Solution:-

The wipers are part of an RC circuit whose time constant can be varied by selecting different values of R through a multiposition switch. As the voltage across the capacitor increases, the capacitor reaches a point at which it discharges and triggers the wipers. The circuit then begins another charging cycle. The time interval between the individual sweeps of the wipers is determined by the value of the time constant.

example 28.9:-

An function of time.

Solution:-

$$T = RC = (8.00 \times 10^5 \Omega)(5.00 \times 10^{-6} \text{F})$$
$$\boxed{T = 4.00 \text{s}}$$

$$Q = (\mathcal{E} - (5.00 \mu\text{F})(12.0 \text{V})) = 60.0 \mu\text{C}$$

$$I_i = \frac{\mathcal{E}}{R} = \frac{12.0 \text{V}}{8.0 \times 10^5 \Omega} = 15.0 \mu\text{A}$$

$$q(t) = (60.0 \mu\text{C})(1 - e^{-t/4.00 \text{s}})$$

$$\boxed{I(t) = (15.0 \mu\text{A})e^{-t/4.00 \text{s}}}$$

example 28.10:-

consider ----- Active fig.

Solution (A):

$$\frac{\phi}{4} = \phi e^{-t/RC}$$

$$\frac{1}{4} = e^{-t/RC}$$

$$-\ln 4 = -\frac{t}{RC}$$

$$t = RC \ln 4 = 1.39 RC$$

$$\boxed{t = 1.39 \tau}$$

(B) The value?

$$u(t) = \frac{q^2}{2C} = \frac{\phi^2}{2C} e^{-2t/RC}$$

$$\frac{1}{4} \frac{\phi^2}{2C} = \frac{\phi^2}{2C} e^{-2t/RC}$$

$$\frac{1}{4} = e^{-2t/RC}$$

$$-\ln 4 = -\frac{2t}{RC}$$

$$t = \frac{1}{2} RC \ln 4$$

$$= 0.639 RC$$

$$\boxed{t = 0.693 \tau}$$

Example 28.11:

A capacitor?

solution:-

$$\Delta U + \Delta E_{\text{int}} = 0$$

$$(0 - U_C) + (E_{\text{int}} - 0) = 0 \rightarrow E_R = U_C$$

$$E_R = \frac{1}{2} C \mathcal{E}^2$$

$$E_R = \frac{1}{2} (5.00 \times 10^{-6} \text{ F}) (800 \text{ V})^2 = \boxed{1.60 \text{ J}}$$

$$P = \frac{dE}{dt} \rightarrow E_R \int_0^\infty P dt$$

$$E_R = \int_0^\infty I^2 R dt$$

$$E_R = \int_0^\infty \left(-\frac{Q}{RC} e^{-t/RC} \right)^2 R dt$$

$$= \frac{Q^2}{RC^2} \int_0^\infty e^{-2t/RC} dt = \frac{\mathcal{E}^2}{R} \int_0^\infty e^{-t/RC} dt$$

$$\boxed{E_R = \frac{\mathcal{E}^2}{R} \left(\frac{RC}{2} \right) = \frac{1}{2} C \mathcal{E}^2}$$