

Name: Maaz Habib

Registration NO: 20PWCSE1952

Total number of pages:6

Final TERM PAPER

Day: MTWTFES

Date: / /

Name: Maaz Habib


Section: C

Reg No: 20PWCSE1952

pg: -1

Q3) Pipelines are ..... circuit shown in fig 2.

Solutions:

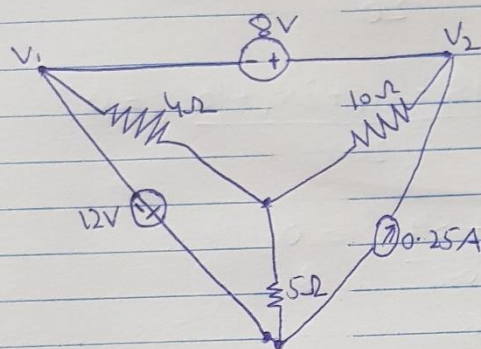

Consider 12V and 8V part a supernode, so it is clear that,

$$V_2 - V_1 = 8V$$

$$\Rightarrow V_2 = V_1 + 8V \quad \text{--- (i)}$$

Also,

$$V_3 - V_1 = 12V$$

$$\Rightarrow V_3 = V_1 + 12V \quad \text{--- (ii)}$$

Now, Applying KCL at Super node which gives,

$$\frac{V_3}{5} + \frac{V_1}{4} + \frac{V_2}{10} = 0 \quad \text{--- (iii)}$$

Substituting Eq (i) and Eq (ii) in Eq (iii) we get,

$$\frac{V_1 + 12V}{5} + \frac{V_1}{4} + \frac{V_1 + 8V}{10} = 0$$

Day: M T W T F S

Date:    /    /   

Name: Maaz Habib  
Reg No: 20PWCSF1952

pg 8-2

Taking L.C.M

$$\frac{4(V_1 + 12) + 5V_1 + 2(V_1 + 8)}{20} = 0$$

$$\frac{4V_1 + 48 + 5V_1 + 2V_1 + 16}{20} = 0$$

$$\frac{11V_1 + 64}{20} = 0$$

$$64 + 11V_1 = 0$$

$$\frac{11V_1}{11} = \frac{-64}{11}$$

$$V_1 = \frac{-64}{11}$$

$$V_1 = -5.818V$$

To find  $V_2$  put  $V_1 = -5.818$  in eq (i)

$$V_2 = V_1 + 8V$$

$$V_2 = -5.818 + 8$$

$$V_2 = 2.180V$$

To find  $V_3$  put  $V_1 = -5.818$  in eq (ii)

$$V_3 = V_1 + 12V$$

$$V_3 = -5.818 + 12$$


$$V_3 = 6.182V$$




Name: MaaZ Habib  
Reg No: 20PWCE1952

(pgt 3)

Q1) Diagram:-

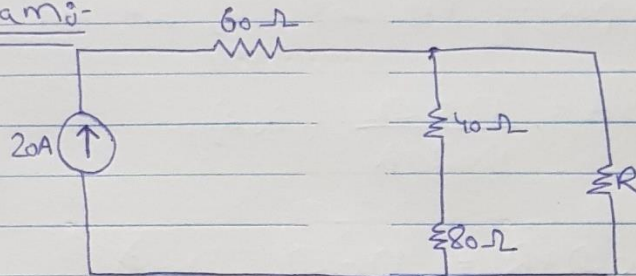

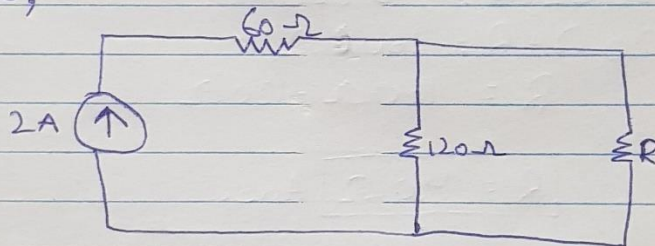Since  $80\Omega$  and  $40\Omega$  are connected in series, some amount of current will flow,  
So,



The parallel equivalent of  $120\Omega$  and  $R$  is;

$$\frac{120R}{120+R}$$

Also,  $60\Omega$  is in series, all  $20A$  will flow through it, Now current flow through  $A$  is, as follows,

$$I_R = \frac{120\Omega}{120\Omega + R} (20A) \quad \text{--- (i)}$$

Since, given in Question that  $5A$  current must flow through  $80\Omega$ , So we need  $R$  to draw  $15A$ ,

So,

$$I_R = 15A \quad \text{--- (ii)}$$

Day M T W T F S

Date.    /    /   

Name + MaaZ Habib  
Reg no + 20PWKSE1952

(pgt 4)

comparing (i) and (ii) we get;

$$15A = \frac{120\Omega}{120\Omega + R} (20A)$$

$$120\Omega + R = \frac{120\Omega \cdot 8}{15A} (20A)$$

$$120\Omega + R = 8(20A)$$

$$120\Omega + R = 160\Omega$$

$$R = 160\Omega - 120\Omega$$

$$\boxed{R = 40\Omega} \text{ Ans.}$$



Name: Maaz Habib

Reg No: 20PWCSE1952

Q2) The growth of cell phones ..... cell phone in your circuit.

Ans:

The circuit for the charger cannot be made due to available components values not matching with required values.

For example:

The required voltage (5V) does not match with the available components of voltage source ( $1.5 \times 2 = 3V$ ).